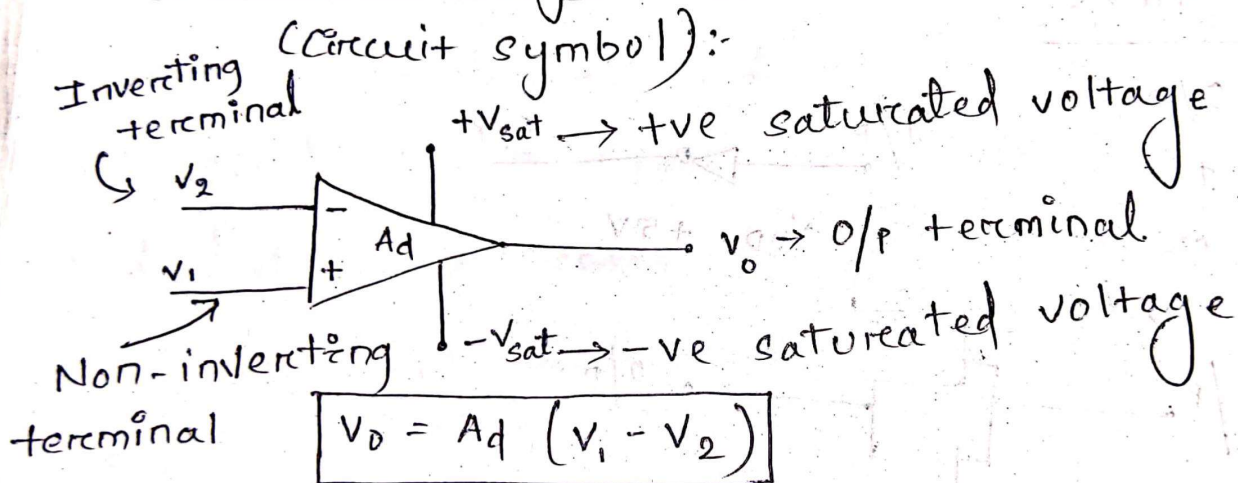



UNIT-IVOp-Amp = Operational Amplifier :-

→ Op-Amp is a high gain differential amplifier with very high i/p ~~imp~~ impedance & very low o/p impedance and used for mathematical operations like addition, subtraction, multiplication, differentiation, integration, exponential operⁿ, log operⁿ etc.

11/11/19Schematic diagram of op-amp :-PIN / IC configuration of OP-amp :-IC no = 741 off set null

Op-amp - 8 pin IC

Non inverting i/p

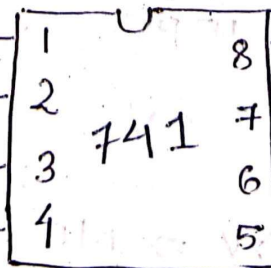 $-V_{sat}$ 


No-connection

 $+V_{sat}$

O/P

off set null


Internal str^u of OP-Amp :-

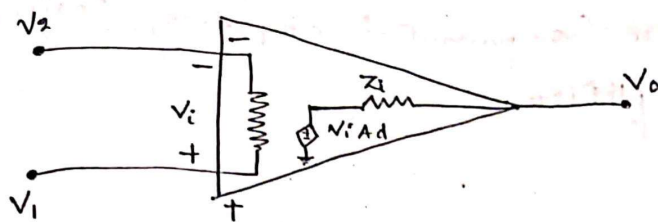

characteristics of ideal op-Amp :-

- i/p impedance is very high ; $Z_i = \infty$
- o/p impedance is very small ; $Z_o = 0$
- voltage gain = very high ;
 $A_d = \infty$
- there is no offset voltage.
- Very high CMRR ; $CMRR = \infty$
(common mode rejection ratio)
- Very low slew rate , slew rate = 0.

Transfer characteristics :-

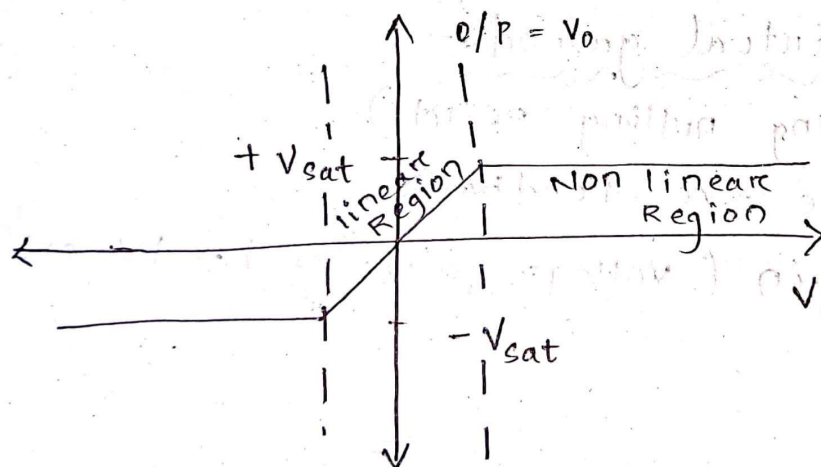

App. of op-Amp in linear region :-

- Inverting amplifier
- Non-inverting amplifier
- Summing amplifier (Adder)
- Subtractor

- Buffer (voltage "follower")
- Log amplifier
- Antilog amplifier (exponential amplifier) } optional
- Differential amplifier
- Differentiate
- Integrator

Virtual Ground :-

13/11/2019

- Earth surface is equipotential surface, so, the potential diff. betⁿ 2 points on the earth's surface is always 0.
- Ground is also equipotential surface in which each point is having 0V potential.
So P.V. betⁿ two points on ground is 0V.
- Current into the ground is max^m. (I_{max})
- In case of virtual ground, P.V. is 0 and current into the virtual ground is 0A.

Condⁿ for virtual ground :-


(Establishing nulling point)

- There must be -ve feedback.
- Very high gain (voltage gain = ∞) $\Rightarrow A_V = \infty$.

OR

- +ve feedback

- Unit gain ($A_V = 1$)

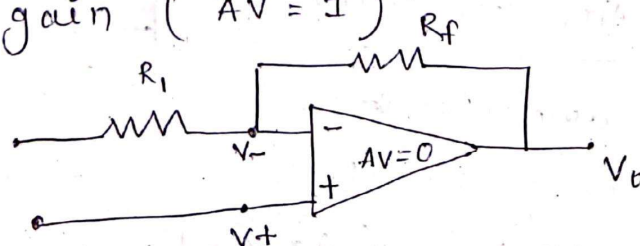

In case of OP-AMP, with -ve feedback and high gain, that exist virtual ground, betⁿ


inverting & non-inverting terminal.

→ In the above fig, $V_+ = V_-$ where,

V_+ → Potential at non-inverting terminal.

V_- → Potential at inverting terminal.

Non-inverting amplifier :-

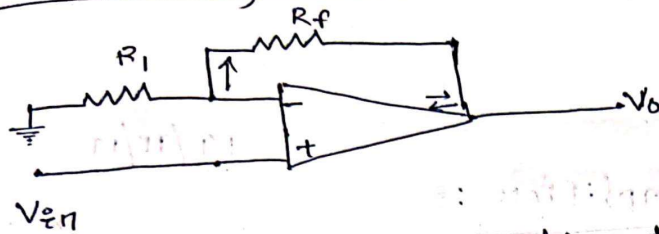


Applying nodal eqⁿ at Inverting terminal :-

$$\frac{V_{in} - 0}{R_1} + \frac{V_{in} - V_o}{R_f} + 0$$

$$V_o = \left(1 + \frac{R_f}{R_1}\right) V_{in}$$

$$\frac{V_o}{V_{in}} = \text{Voltage gain} = \left(1 + \frac{R_f}{R_1}\right)$$

Q:-

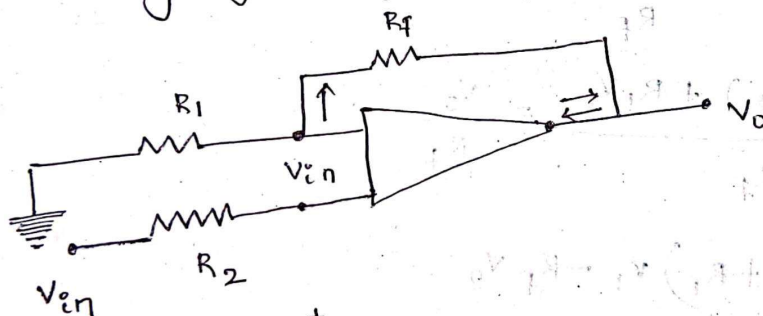


calculate the output.

$$\frac{V_{in} - 0}{R_1} + \frac{V_{in} - V_o}{R_f} + 0 = 0$$

$$V_o = \left(1 + \frac{R_f}{R_1}\right) V_{in}$$

Inverting amplifier :-

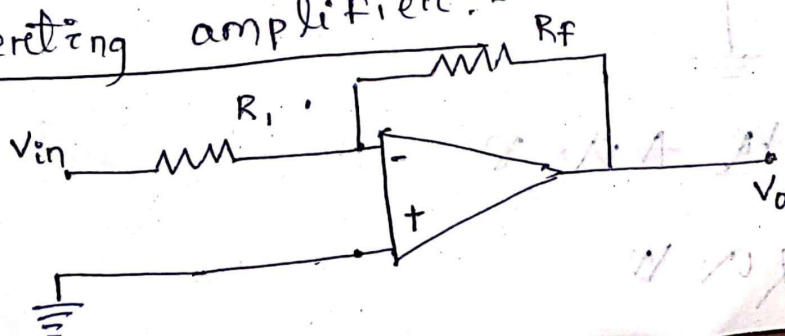

$$\frac{0 - V_{in}}{R_f} + \frac{V_{in} - V_{in}}{R_f} + 0 = 0$$


$$V_o = \left(1 + \frac{R_f}{R_i} \right) V_{in}$$

$$\frac{0 - V_{in}}{R_i} + \frac{0 - V_i}{R_f} = 0$$

$$V_o = - \frac{R_f}{R_i}$$

14/11/19

Differential Amplifier :-

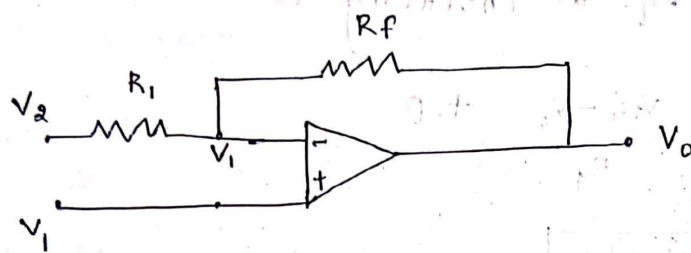


Applying nodal at inverting terminal

$$\frac{V_1 - V_2}{R_i} + \frac{V_1 - V_o}{R_f} + 0 = 0$$

$$\Rightarrow \frac{R_f(V_1 - V_2) + R_i V_1}{R_i R_f} = \frac{V_o}{R_f}$$

$$\Rightarrow V_o = \frac{(R_f + R_i)V_1 - R_f V_2}{R_i}$$

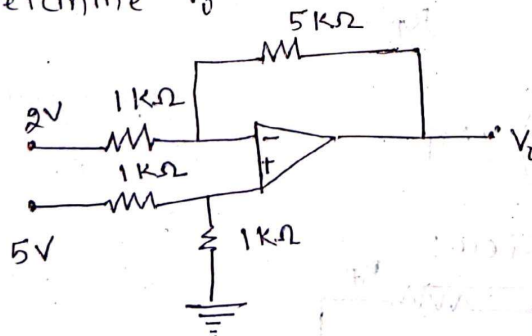Q:- Determine V_o for the following circuit.



$$\frac{5 - V_o}{1} + \frac{5 - V_o}{5} + 0 = 0$$

$$5 + \left(1 - \frac{V_o}{5} \right) + 0 = 0$$

$$V_+ = \frac{5 \times 1k\Omega}{1k\Omega + 1k\Omega} = \frac{5}{2} V = 2.5 V$$


$$V_- = \frac{5}{2} V = 2.5 V$$

Applying nodal at inverting terminal,

$$\frac{2.5 - 2}{1k\Omega} + \frac{2.5 - V_0}{5k\Omega} + 0 = 0$$

$$\Rightarrow V_0 = 5 V$$

Summing Amplifier :- (Adder)

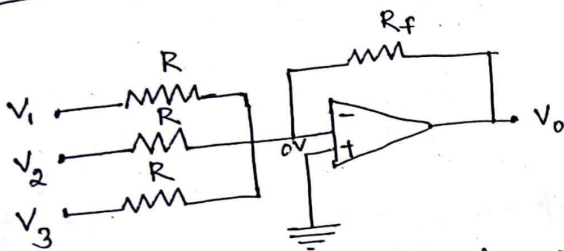

$$\frac{V_1 - V_2}{R} + \frac{V_1 - V_0}{R_f}$$


Apply nodal at inverting terminal,

$$\frac{0 - V_0}{R_f} + \frac{0 - V_1}{R} + \frac{0 - V_2}{R} + \frac{0 - V_3}{R} + 0 = 0$$

$$\Rightarrow \frac{0 - V_0}{R_f} + \left(\frac{-1}{R} \right) (V_1 + V_2 + V_3) = 0$$

$$\Rightarrow V_0 = -\frac{R_f}{R} (V_1 + V_2 + V_3)$$


Buffer / voltage follower:-

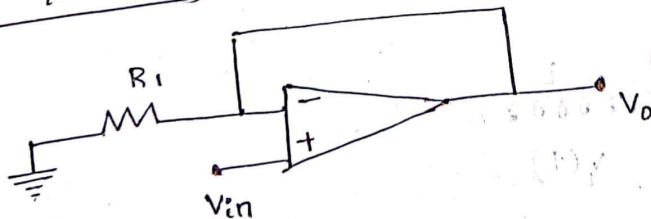

$$V_0 = V_{in}$$

$$\text{gain} = A_V = 1$$


Subtractor Amplifier:-

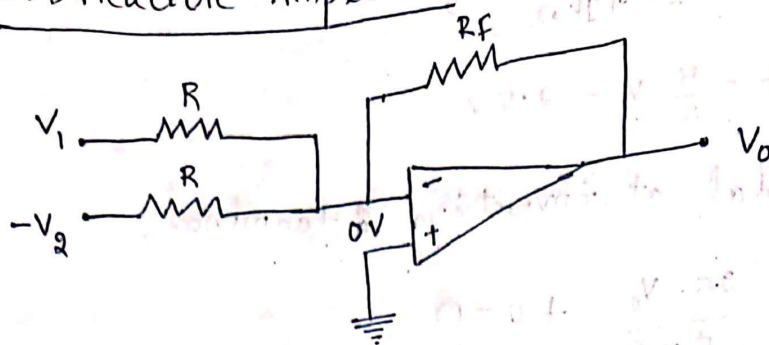

$$\frac{0-V_0}{R_f} + \frac{0-V_1}{R} + \frac{0+V_2}{R} = 0$$

$$V_0 = -\frac{R_f}{R} (V_1 - V_2)$$

Note-1

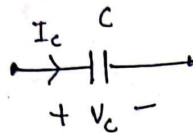

$$I_c = C \frac{dV}{dt}$$

$$\Rightarrow C \frac{dV}{dt} = i_c$$


$$\Rightarrow \frac{dV_c}{dt} = \frac{1}{C} i_c$$

$$\Rightarrow \int dV_c = \frac{1}{C} \int i_c dt$$

$$\Rightarrow V_c(t) = \frac{1}{C} \int_{-\infty}^t i_c(t) dt$$

Note-2


Inductor (L)

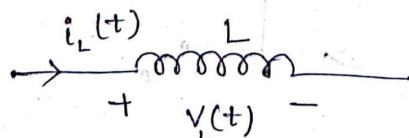

$$V_L(t) = L \frac{di_L(t)}{dt}$$

$$i_L(t) = \frac{1}{L} \int_{-\infty}^t V_L(t) dt$$

Integrator :-

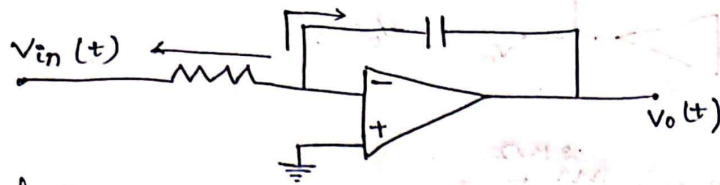


Applying nodal at inverting terminal,

$$\frac{0 - v_{in}(t)}{R} + C \frac{d}{dt} (0 - v_o(t)) + 0 = 0$$

$$\Rightarrow -C \frac{d v_o(t)}{dt} = \frac{v_{in}(t)}{R}$$

$$\Rightarrow \frac{d v_o(t)}{dt} = -\frac{1}{RC} v_{in}(t)$$

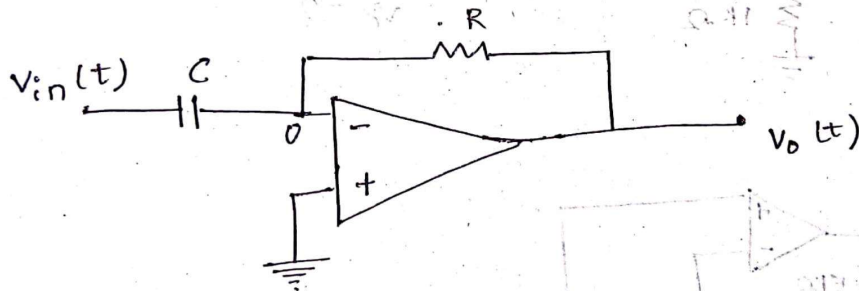
$$\Rightarrow v_o(t) = -\frac{1}{RC} \int_{-\infty}^t v_{in}(t) dt$$




$$C \frac{d}{dt} (0 - v_{in}(t)) + \frac{0 - v_o(t)}{R} + 0 = 0$$

$$\Rightarrow v_o(t) = -RC \frac{d}{dt} v_{in}(t)$$


Q:-1)

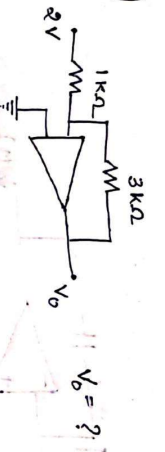


Q:-2)

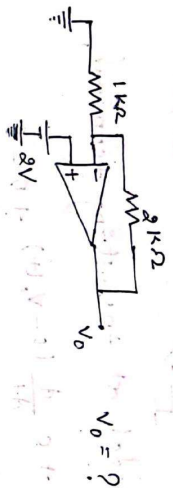


Q:-3)

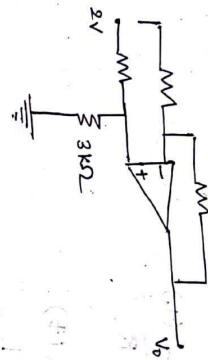


Q:-4)

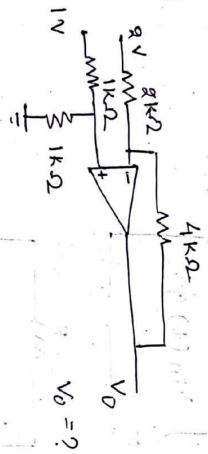

Q:-5)

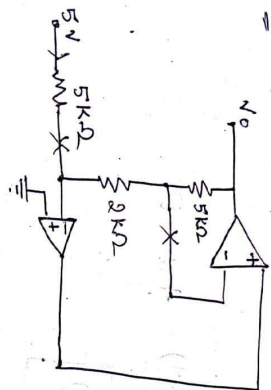

Q:-6)

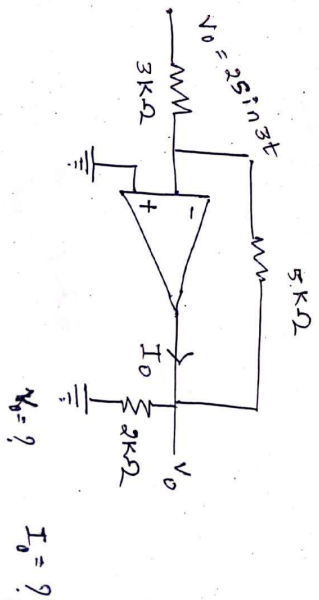

1) Applying nodal at inverting terminal,

$$\frac{0-V_0}{R_F} + \frac{0-V_1}{R} + 0 = 0$$

$$\Rightarrow V_0 = \frac{-R_F}{R_1} (V_1 - V_2)$$

$$\Rightarrow V_0 = -\frac{3}{1} (2-0)$$

$$\Rightarrow \boxed{V_0 = -6V}$$

2) Applying nodal at inverting terminal,

$$V_1 = \frac{1 \times 2}{2+1} = \frac{2}{3} = 0.6V$$

$$V_1 = \frac{1}{2} V = 0.5V$$

$$\frac{0.5-2}{2} + \frac{0.5-V_0}{4} = 0 \Rightarrow \frac{-3+0.5-V_0}{4} = 0$$

$$\Rightarrow -3+0.5-V_0 = 0 \Rightarrow \boxed{V_0 = -2.5V}$$

$$2) \frac{2-0}{1K} + \frac{2-V_0}{2K} + 0 = 0$$

$$\Rightarrow V_0 = \left(1 + \frac{2}{1}\right) \times 2 = 3 \times 2 = 6V$$

$$\Rightarrow \boxed{V_0 = 6V}$$

$$3) V_1 = \frac{2 \times 3K}{3K+3K} = 1V$$

$$V_0 = \frac{1-0}{6K} + \frac{1-V_0}{6K} + 0 = 0$$

$$\Rightarrow \boxed{V_0 = 2V}$$

$$5) \text{ Hence ; } \frac{0-5}{5K} + \frac{0-V_0}{7K} + 0 = 0 \Rightarrow 5V_0 = -35$$

$$\Rightarrow \frac{-35-5V_0}{35} = 0 \Rightarrow \boxed{V_0 = -7V}$$

$$e) \frac{0 - V_{in}}{3K} + \frac{0 - V_o}{5K} + 0 = 0$$

$$\Rightarrow V_o = -\frac{5}{3} V_{in}$$


$$= -\frac{10}{3} \sin 3t \text{ V}$$

Applying KVL:

$$-I_o + \frac{V_o - 0}{5K} + \frac{V_o - 0}{2K} = 0$$


$$\Rightarrow \frac{V_o}{5K} + \frac{V_o}{2K} = I_o$$
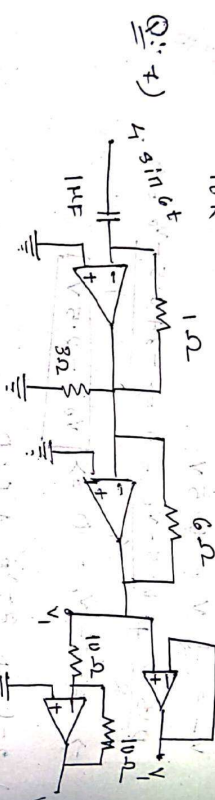
$$\Rightarrow I_o = \frac{7V_o}{10K} = -\frac{7}{3} \sin 3t \text{ mA}$$



Find relationship betⁿ V_1 & V_2 .

Q: 8)

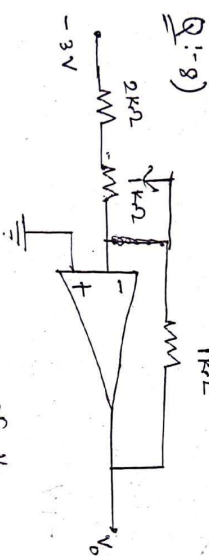

Find the range of V_o .

Ans:-


$$7) 0 - V_2 + \frac{0 - V_1}{10} = 0$$

$$\Rightarrow \frac{-V_2}{10} = \frac{V_1}{10}$$



$$\Rightarrow V_1 = -V_2$$

$$\text{or } V_2 = -V_1$$
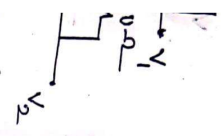
$$\begin{aligned}
 \phi) V_0 &= -\frac{1}{2} \times 2 = -1 \text{ V} \\
 V_1 &= -\frac{1}{2} \times -9 = \frac{9}{2} = 1.5 \text{ V}
 \end{aligned}$$



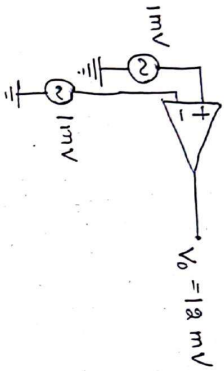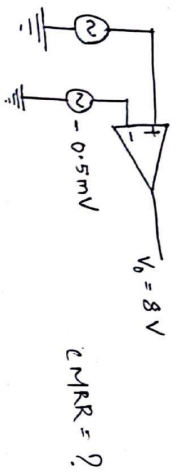Q: For an experimental set up, which op-amp is shown below:-



$$CMRR = \frac{A_d}{A_c}$$

$$A_d = \frac{V_{o,d}}{V_{i,d}} = \frac{8V}{0.5 + 0.5mV} = 8000$$

$$A_c = \frac{V_{oc}}{\left(\frac{V_1 + V_2}{2}\right)} = \frac{12mV}{1mV} = 12$$

$$CMRR = \frac{8000}{12} \rightarrow \text{Absolute state}$$

$$CMRR|_{dB} = 20 \log_{10} \left(\frac{8000}{12} \right) \text{ dB}$$

Q: Determine the o/p voltage of op-amp for the i/p voltage $V_{i1} = 200\mu V$, $V_{i2} = 140\mu V$. The amplifier has the differential gain $A_d = 6000$ and $CMRR$ is 800.

$$V_{i1} = 200\mu V$$

$$V_{i2} = 140\mu V$$

$$CMRR = 200$$

$$A_d = 6000$$

$$V_{id} = V_{i1} - V_{i2} = 200 - 140 = 60 \mu V$$

$$V_{ic} = \frac{V_{i1} + V_{i2}}{2} = 140 \mu V$$

$$CMRR = \frac{A_d}{A_c}$$

$$\Rightarrow 200 = \frac{6000}{A_c}$$

$$\Rightarrow A_c = 30$$

$$A_d = \frac{V_{od}}{V_{id}} = \frac{V_{od}}{60 \mu V}$$

$$\Rightarrow V_{od} = 6000 \times 60 \mu V = 360 mV$$

$$A_c = \frac{V_{oc}}{V_{ic}} = \frac{V_{oc}}{140 \mu V}$$

$$\Rightarrow V_{oc} = 30 \times 140 \mu V = 5100 = 5.1 mV$$


$$V_D = V_{od} + V_{oc}$$

$$= 360 + 5.1 = 365.1 mV$$


Slew Rate:-

This is the characteristics of op-amp and defined as max^m rate of change of o/p for any applied input.

Mathematically, $SR \triangleq \left. \frac{dV_o}{dt} \right|_{max} \left(\frac{V_{olt}}{\mu s} \right)$

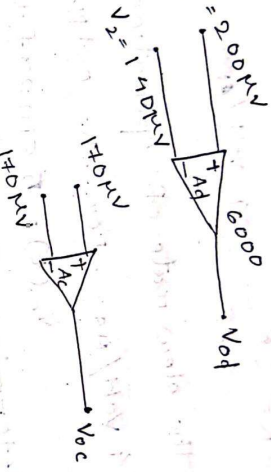

Q:- Determine the slew rate:

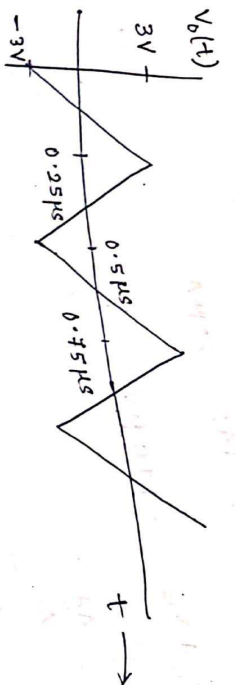

$$SR \triangleq \frac{6}{0.25} = 24 \text{ Volt}/\mu\text{s}$$

Q:- The slew rate of operational amplifier is 24 Volt/ μ s. For the output ~~of~~ $V_o(t) = 5 \sin 2\pi f_o t$ V.

Determine the frequency of o/p signal or

Op-Amp.

$$SR \triangleq = 24 \text{ Volt}/\mu\text{s}$$



$$sl = \left. \frac{dV_o}{dt} \right|_{\text{max}}$$

$$= 10\pi f_o \cos 2\pi f_o t \Big|_{\text{max}}$$

$$24 \sqrt{10} = 10\pi f_o$$

$$f_o = \frac{24}{10\pi} \times 10^6 \text{ Hz} = \frac{24}{\pi} \text{ MHz}$$

Significance of slew rate:-

→ It is used to calculate the frequency of o/p signal and also used to calculate the max ~~sw~~ swing in o/p signal.

Write the block diagram of OP-AMP:-

